

## **Basic Electronics Laboratory**

### TABLE OF CONTENTS

S No.	Name of the Experiment	Page No.
1.	To analyze and design a resistive network.	
2.	To analyze and study the time response of RC and RL circuits.	
3.	To analyze and study the frequency response of RC and RL circuit.	
4.	Designing and analyzing an inverting and non- inverting mode Amplifier using Op-Amp.	
5.	To analyze and design an adder and scalar circuit using IC 741.	
6.	To analyze and design a band pass circuit.	
7.	To study and analyze the basic logic gates and universal gate.	
8.	To analyze and design, digital circuits used for performing basic arithmetic operation as addition and subtraction.	
9.	To analyze and design a Sequential Circuits (Flip Flops and Latches).	