

Analog Electronics Laboratory

TABLE OF CONTENTS

S. No.	Name of the Experiment	Pages
1.	To study the clipping and clamping functions found in circuits using diodes. The designs that are required to be implemented and built are the various diode clipper and clamper circuits.	8
2.	To analyze basic building blocks of a DC Power Supply, and design Regulated Power Supply.	6
3.	To measure the I-V characteristics of different color LED, and measure some of the many important characteristics of the Photo Diode & Infrared LED.	5
4.	To find β (common emitter current gain) of a particular transistor by measuring different values of base current (I_B) with the corresponding values of collector current (I_C). Also, design a basic switch and digital gates using BJT.	4
5.	To design and analyze different aspects of a Self-Biased Common Emitter Amplifier using Bipolar Junction Transistor (BJT).	5
6.	To calculate the voltage gain and frequency response of RC Coupled amplifier.	4
7.	To explore the basic concepts of oscillators and design of sine wave oscillators using transistor and Op-Amp. Also, design Wien Bridge oscillator using Op-amp (741) and RC-Phase shift oscillator using bipolar junction transistor (BC-547).	5
8.	To study the astable and monostable modes of the 555 timer Integrated Circuit (IC).	5
9.	To understand the basic fundamentals of Analog-to-Digital Converters (ADC) and Digital-to Analog Converters (DAC) using different techniques, namely counter and the R-2R ladder.	4